

Experiment 2: Non-Ideal Op-Amps, Pre-Lab Worksheet

Student name:

Lab group:

2. Pre-Lab

2.1. Introduction to LTSpice

What feedback resistor value gave that?
What kind of circuit are you simulating?
Attach the plot to your pre-lab report.

2.2. DC Open Loop Transfer Characteristic

Open loop gain A_0 :
Voltage offset $V_{\text{offset}} \equiv -V_{\text{shift}}$:
Plot of the DC Open Loop Transfer Characteristic:

2.3. Slew Rate in Unity Gain Configuration

Slew Rate:

Is it reasonable based on the datasheet?

Plot of V_{out} and V_{in} versus time:

Is the slew rate different for rising and falling voltages?

2.4. Gain and Bandwidth in Unity Gain Configuration

Gain A_0 :

Bandwidth f_{3dB} :

Plot of the gain vs frequency (log-log scale):

For 100KHz input at what amplitude the amplifier will start slewing?

Plot of the input and the output for this amplitude, and for twice this amplitude, on the same plot:

2.5. Gain and Bandwidth in Non-Inverting Amplifier Configuration

R=10k Ω	Gain A0:
	Bandwidth f3dB:
R=100k Ω	Gain A0:
	Bandwidth f3dB:

Plot of magnitude response of the voltage gain in log-log scale for the two non-inverting amplifier circuits and the circuit from Problem 2.5 on the same plot:

At approximately what frequency and gain do the three curves intersect on the plot? What does this mean?

With R=10k Ω , for 10KHz input at what amplitude the amplifier will start slewing?

Plot of the input and the output for this amplitude, and for twice this amplitude, at the same plot: